

**CS 2200**

**Lab 3**

# Today's Topic:

## Datapath and Buses



# Announcements

- **Project 1** due **Sunday, September 17 @ 11:59 PM**
- **Homework 1** due tonight **@ 11:59 PM** as per extension
- **Homework 2** releases tonight, due **Tuesday, September 12 @ 11:59 PM**
- **Test 1** is next **Wednesday, September 13** in lab
  - **Bring your buzzcard!!**

# Test Logistics

- 60 minutes (First hour of lab)
- Open book, open note, open google
  - No AI use or communication
  - Download all notes as PDF (No text editors open)
  - No Honorlock (this time)
- Everything up to and including datapath (No FSM/microcontroller)
- Bring buzzcard for attendance
- ODS: Testing center on 9/13, 9/14


# Exercise: ALU Implementation

We want to implement an ALU that can compute all sorts of **bit shifts**. Here's what we want to support:

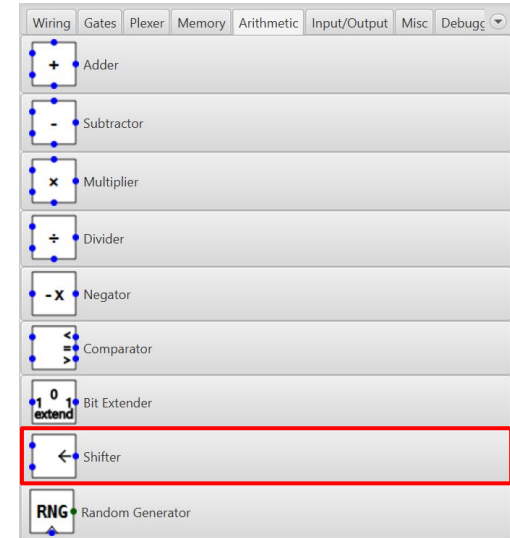
1. Left shift
2. Logical right shift (fill with zeros)
3. Arithmetic right shift (fill with MSB)
4. Left rotate

Need a refresher on what these operations entail? [This](#) might help.

Spend **10-15 minutes** implementing this in CircuitSim. Take a look at the **Shifter** component. Assume **16-bit** architecture.




## Answer: ALU Implementation

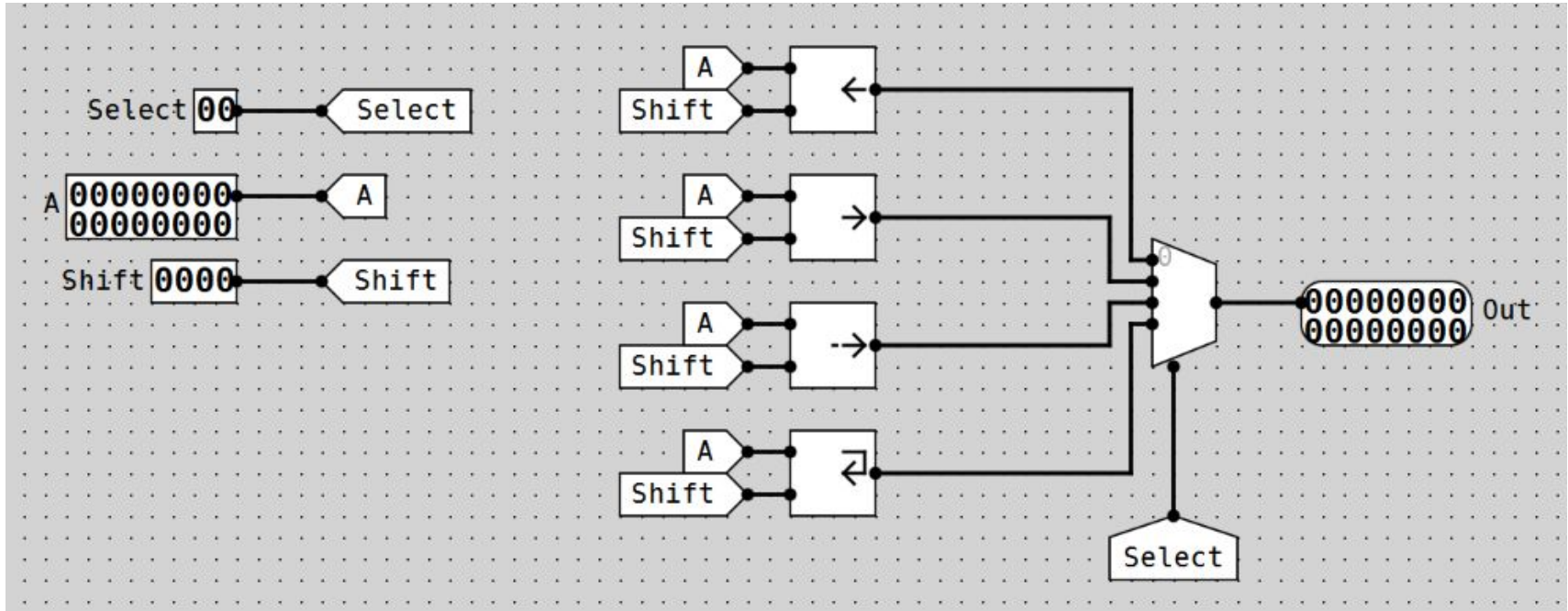
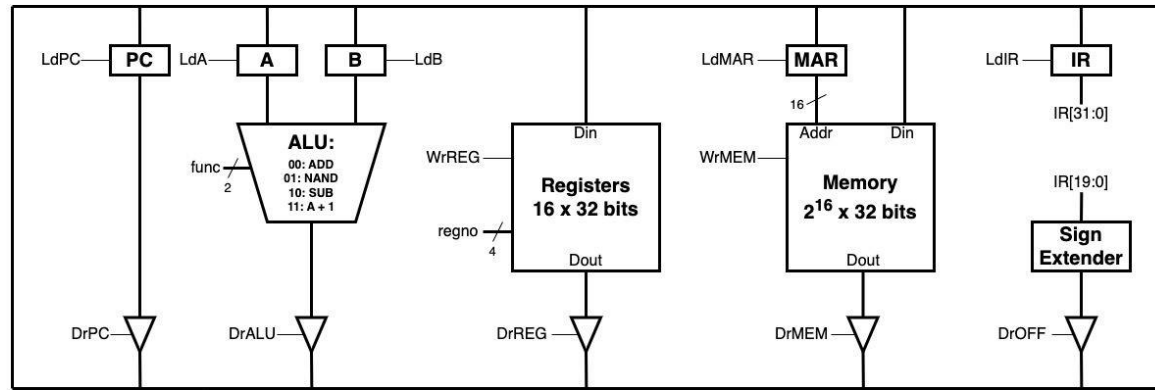
# Exercise: Implement NAND on LC-2200 datapath

How many cycles and what control signals are required to implement NAND on the LC-2200 datapath? Spend **5 minutes** tracing each cycle.



Anatomy of an R-type instruction.



Table 4: Register Selection Map

RegSelHi	RegSelLo	Register
0	0	RX (IR[27:24])
0	1	RY (IR[23:20])
1	0	RZ (IR[3:0])
1	1	unused

# Implementing NAND

1. Store register Y in A
2. Store register Z in B
3. NAND A and B and store in register X


## R-type instructions (add, nand):

bits 31-28: opcode  
 bits 27-24: reg X (destination)  
 bits 23-20: reg Y (source)  
 bits 19-4: unused (should be all 0s)  
 bits 3-0: reg Z (source)



Table 4: Register Selection Map


RegSelHi	RegSelLo	Register
0	0	RX (IR[27:24])
0	1	RY (IR[23:20])
1	0	RZ (IR[3:0])
1	1	unused

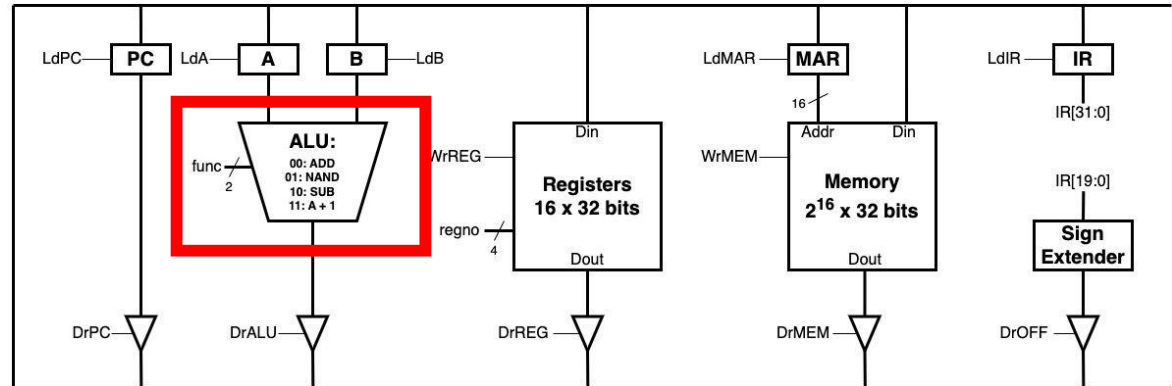




# NAND Cycle 1: $R_y \rightarrow A$

What signals need to be asserted?

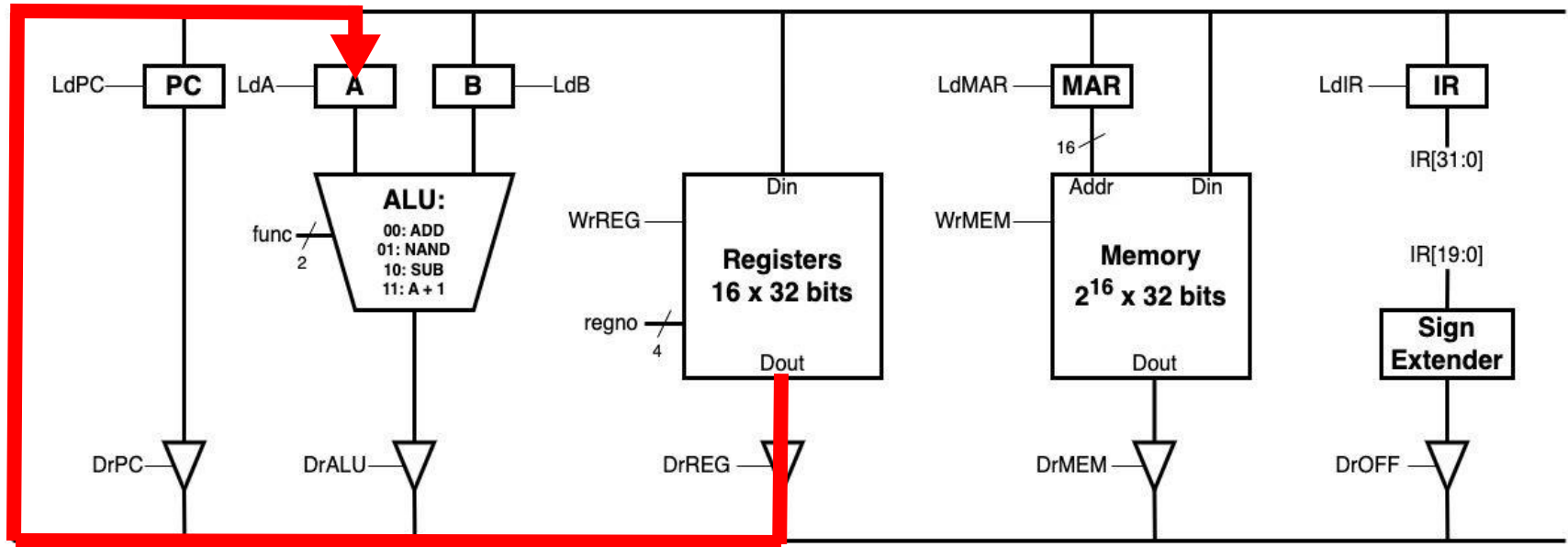


# NAND Cycle 1: Ry $\rightarrow$ A

DrReg, LdA, RegSel = 01

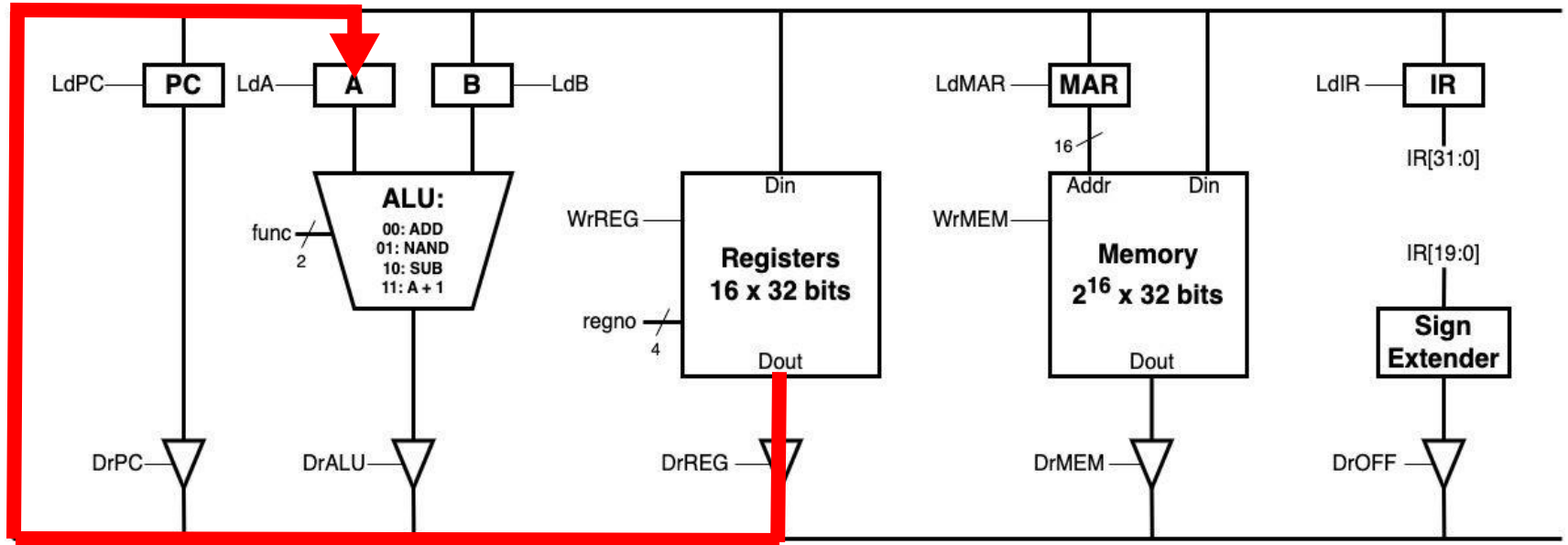


# NAND Cycle 2: Rz → B

What signals need to be asserted?

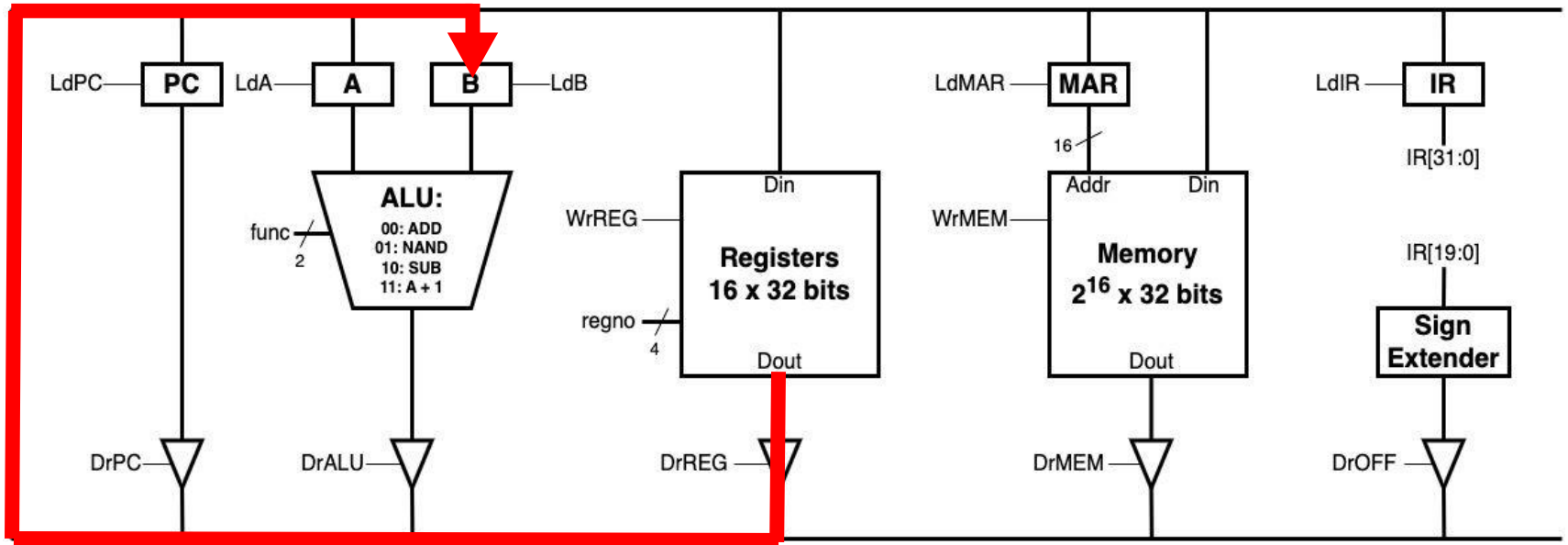


# NAND Cycle 2: Rz → B

DrReg, LdB, RegSel = 10

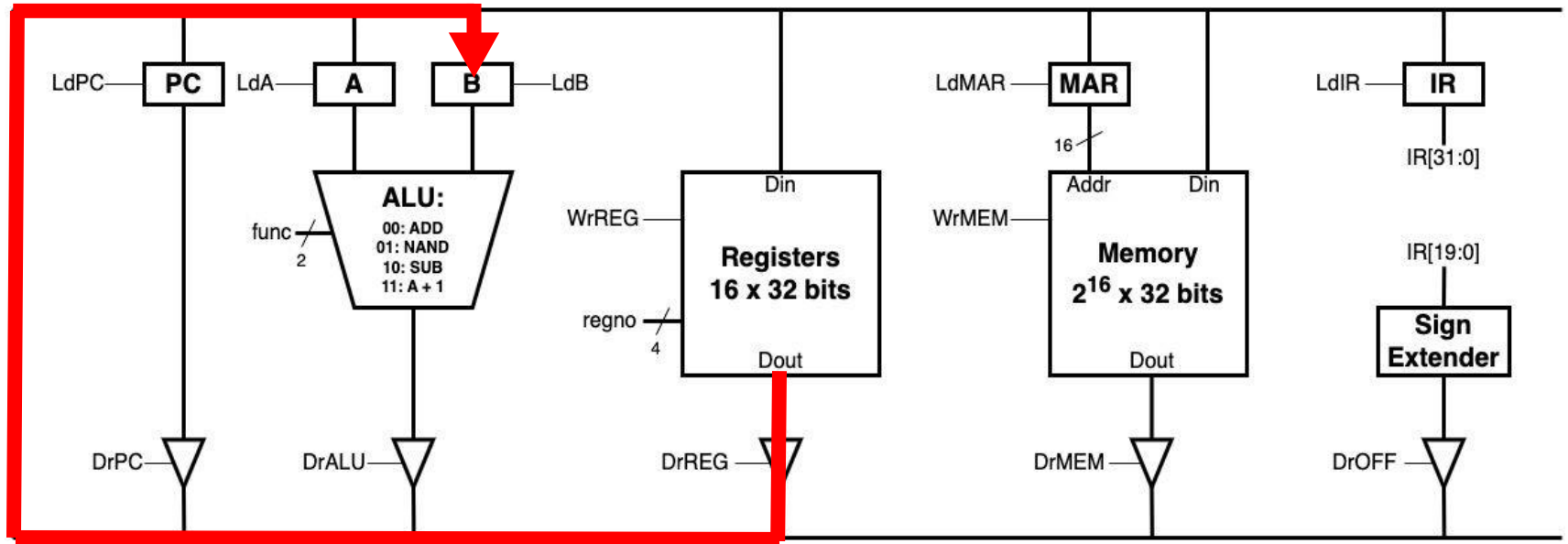


# NAND Cycle 3: ALUOut $\rightarrow$ Rx

What signals need to be asserted?

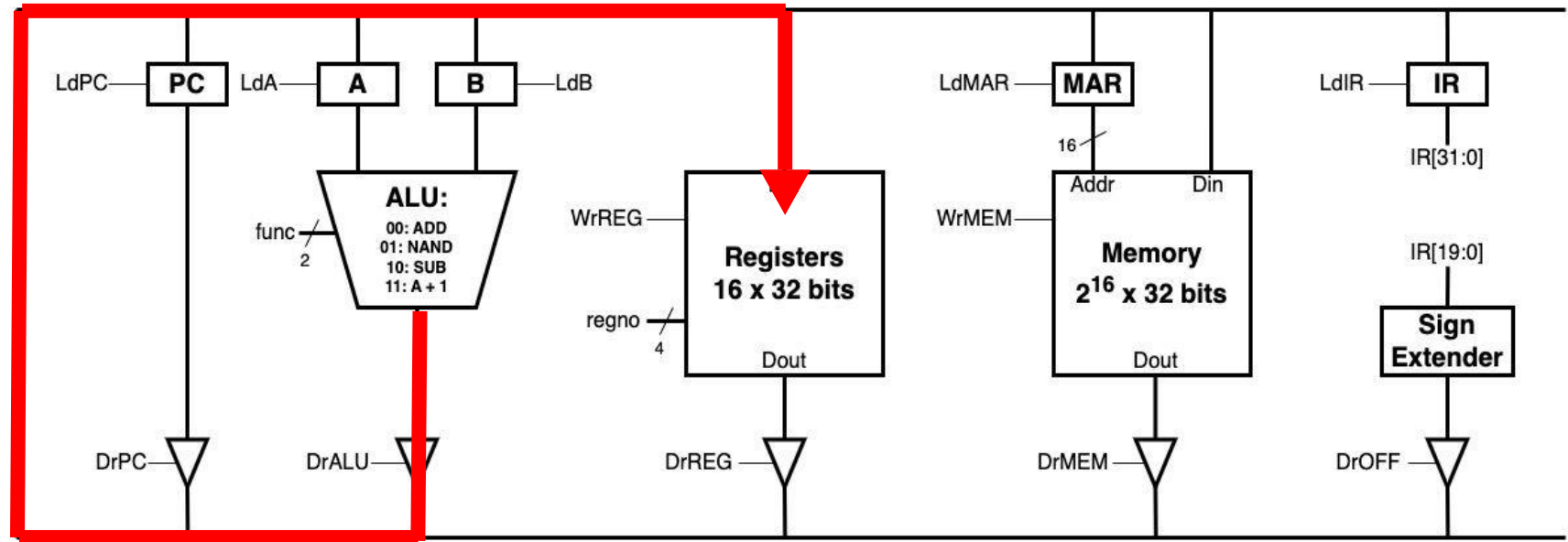

# NAND Cycle 3: ALUOut $\rightarrow$ Rx

DrALU, WrREG, func = 01, RegSel=00



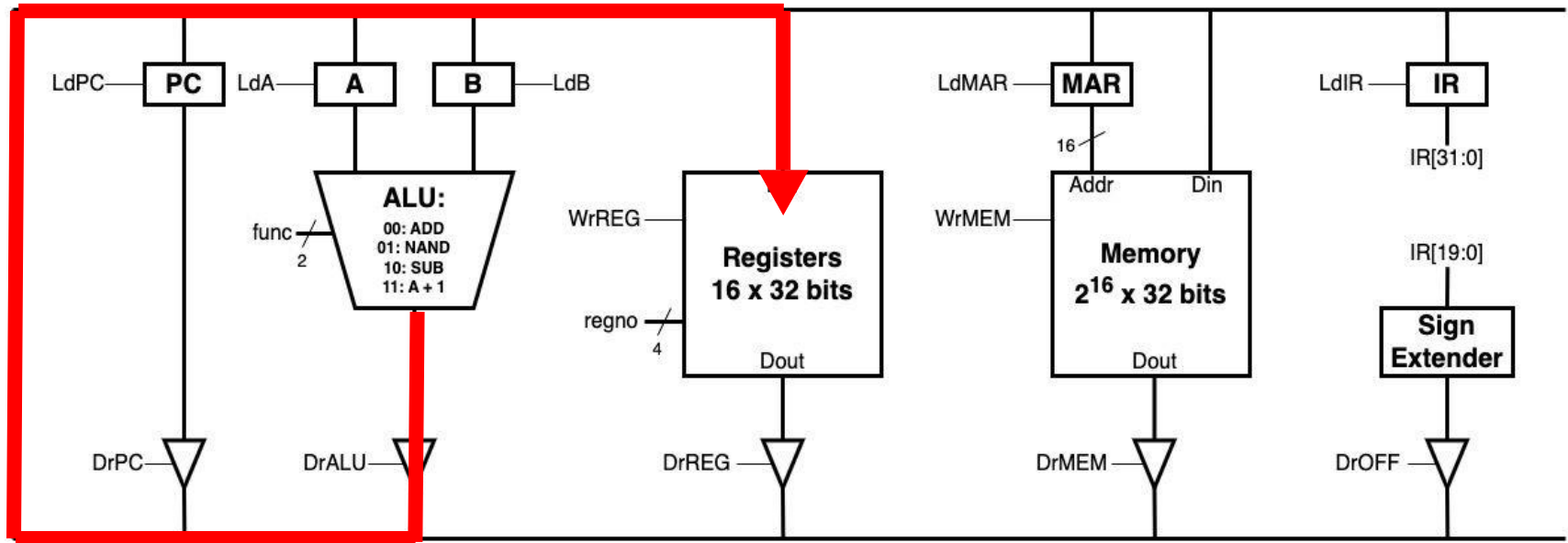


# Implementing NAND

**Cycle 1:** DrReg, LdA, RegSel = 01


**Cycle 2:** DrReg, LdB, RegSel = 10

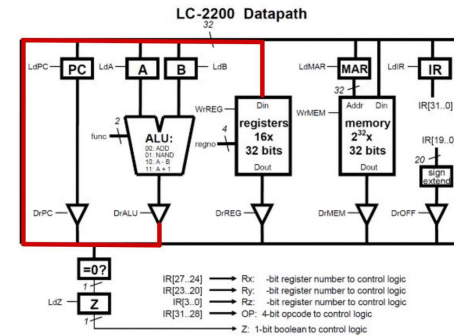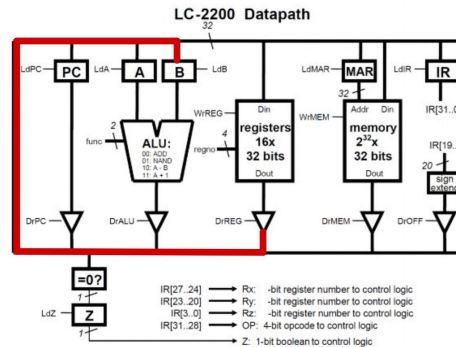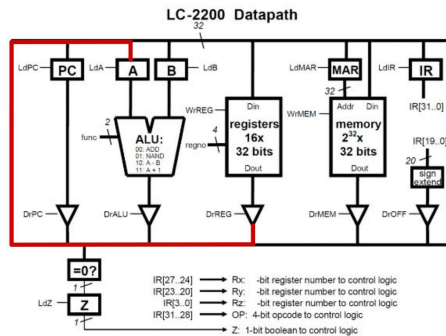**Cycle 3:** DrALU, WrReg, func = 01, RegSel=00


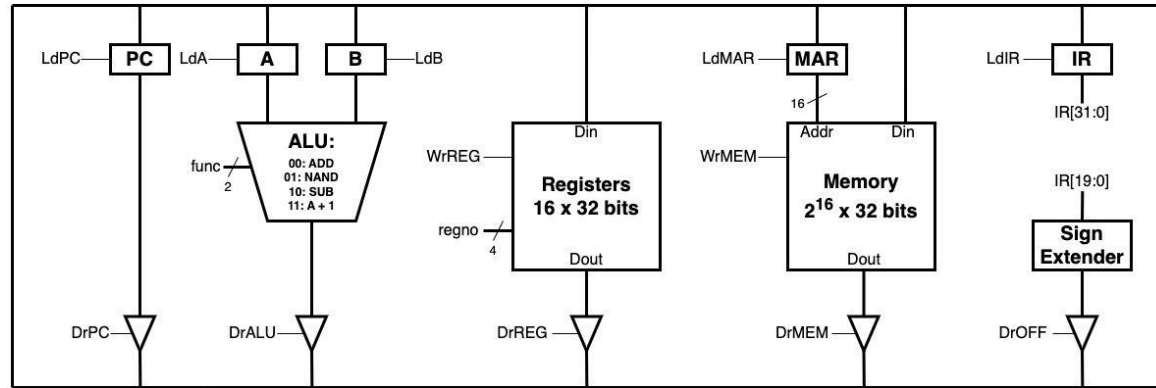
# Exercise: Implement JALR on LC-2200 datapath

How many cycles and what control signals are required to implement JALR on the LC-2200 datapath? Spend **5 minutes** tracing each cycle.



Anatomy of a J-type instruction.

 


Table 4: Register Selection Map

RegSelHi	RegSelLo	Register
0	0	RX (IR[27:24])
0	1	RY (IR[23:20])
1	0	RZ (IR[3:0])
1	1	unused



# Implementing JALR

Store  $PC + 1$  in  $R_y$


Branch to the address in  $R_x$

## J-type instructions (jalr):<sup>6</sup>

bits 31-28: opcode  
 bits 27-24: reg X (target of the jump)  
 bits 23-20: reg Y (link register)  
 bits 19-0: unused (should be all 0s)


Table 4: Register Selection Map

RegSelHi	RegSelLo	Register
0	0	RX (IR[27:24])
0	1	RY (IR[23:20])
1	0	RZ (IR[3:0])
1	1	unused

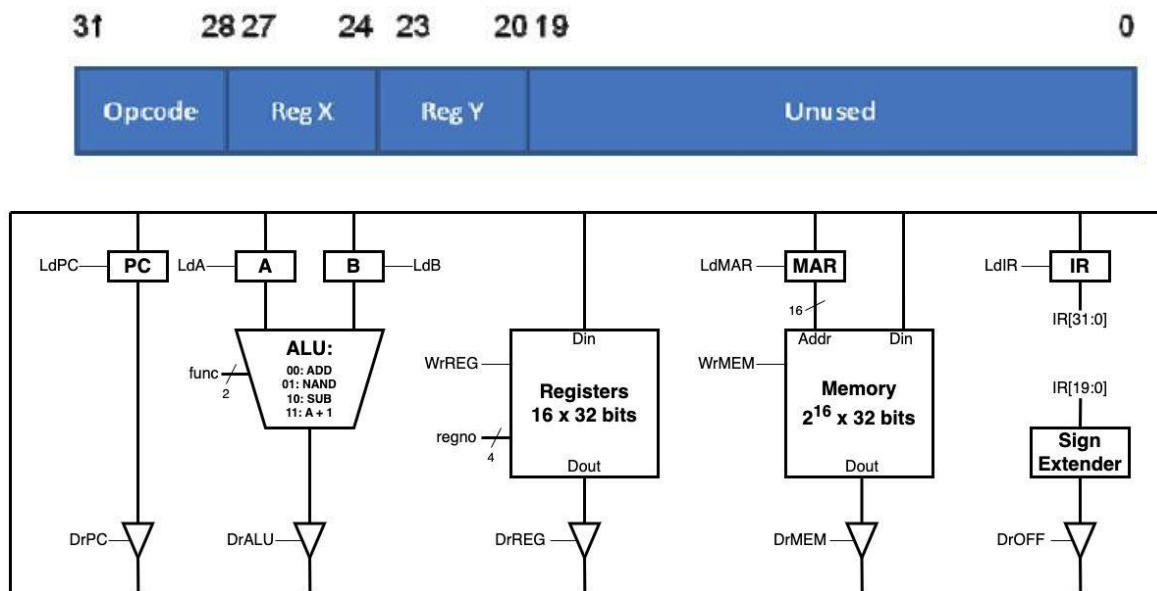


# JALR Cycle 1: PC $\rightarrow$ Ry

What signals need to be asserted?

 


# JALR Cycle 1: PC $\rightarrow$ Ry

DrPC, WrREG, RegSel = 01

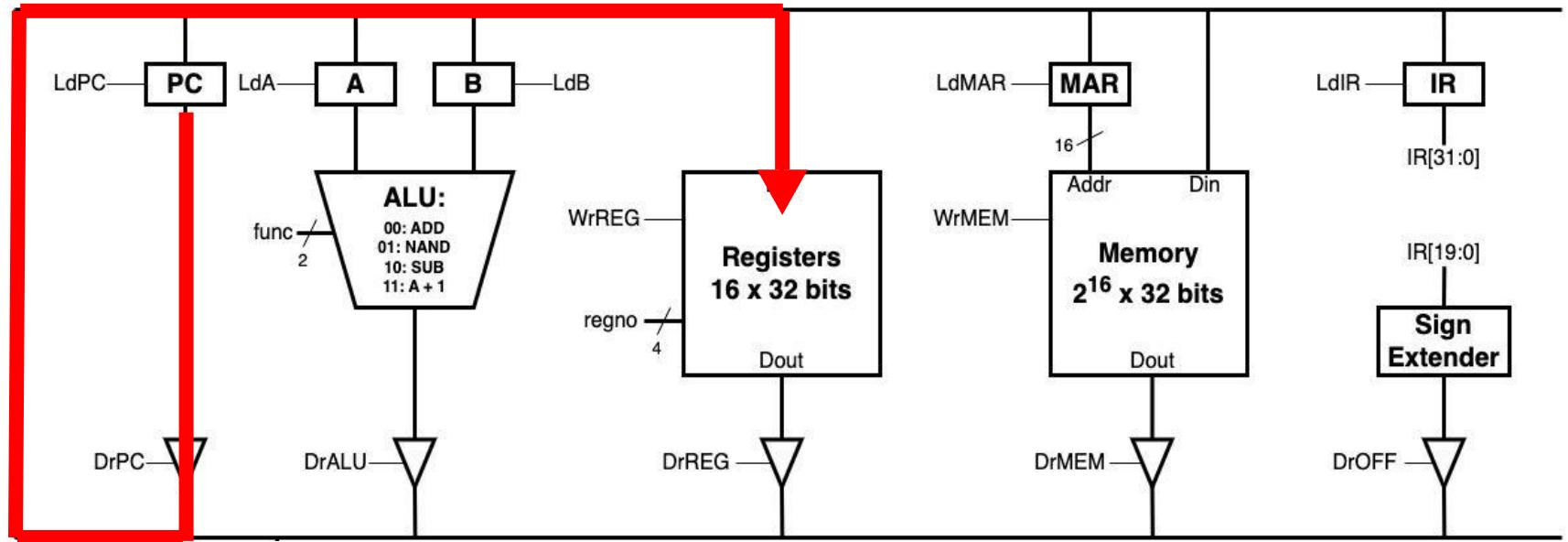


# JALR Cycle 2: Rx $\rightarrow$ PC

What signals need to be asserted?

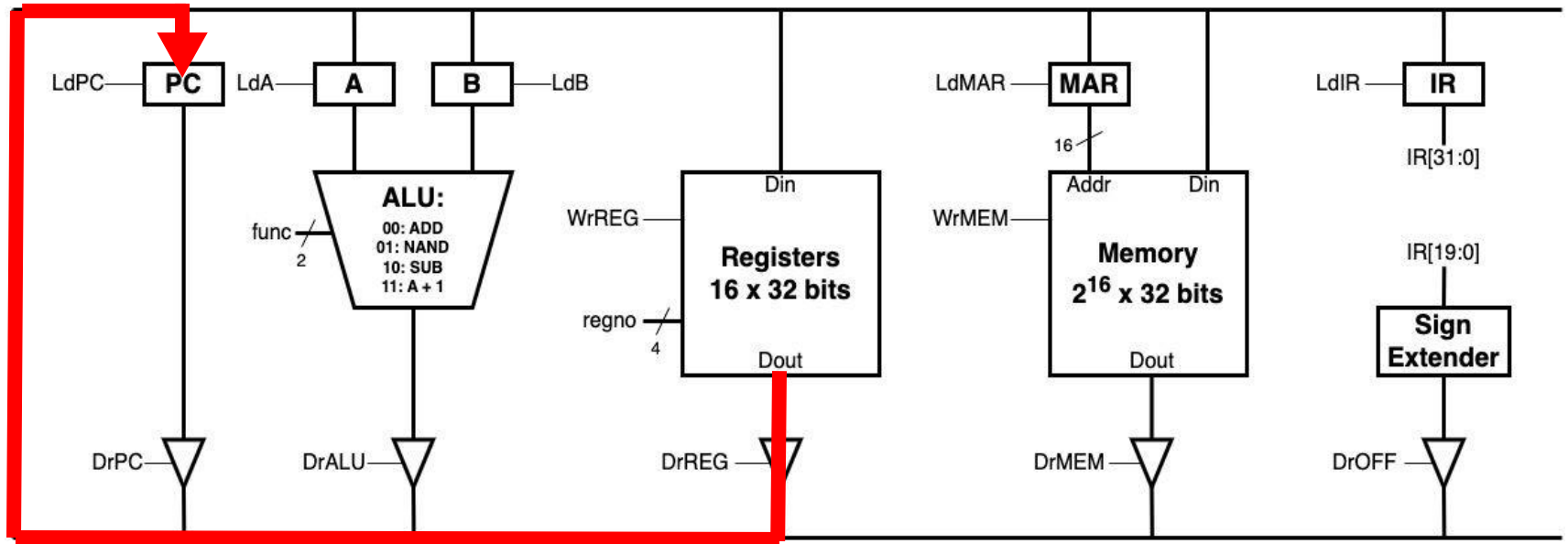

# JALR Cycle 2: Rx → PC

DrREG, LdPC, regSel = 00

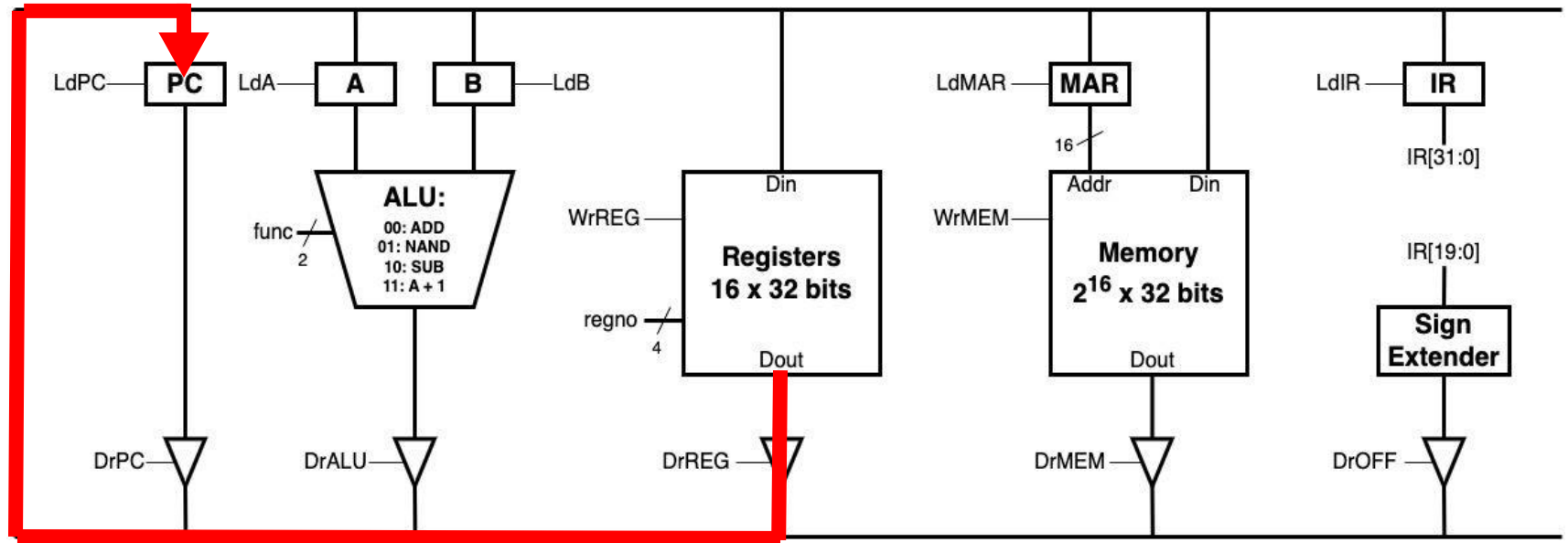

# Implementing JALR



$R_y \leftarrow PC + 1$  \*

$PC \leftarrow R_x$

**Cycle 1:** DrPC, WrREG, regSel = 01


**Cycle 2:** DrREG, LdPC, regSel = 00

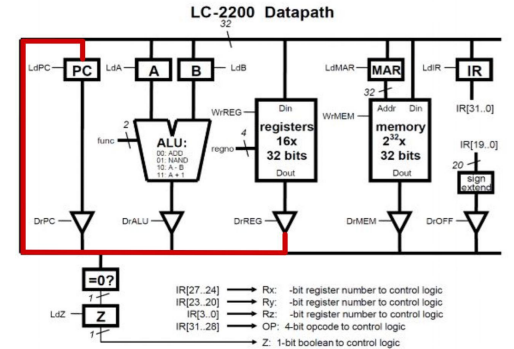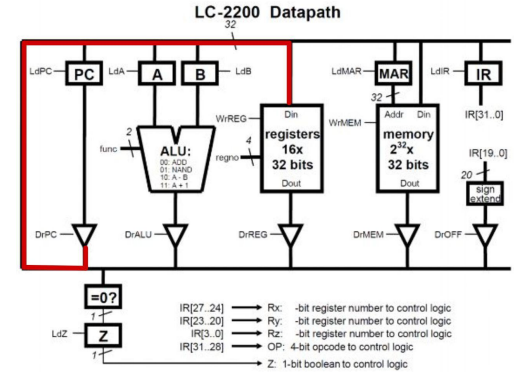**Note:** By the time an instruction executes, the PC has *already* been incremented! We don't have to do that again during the execution macrostate.


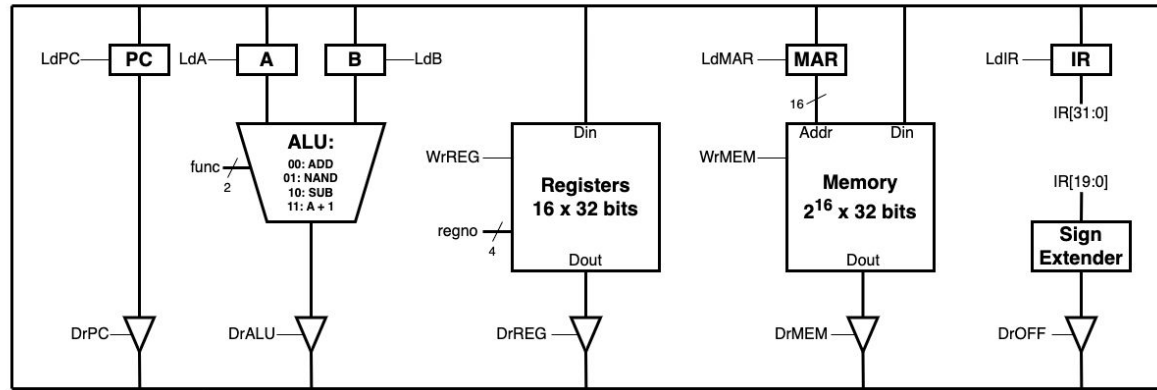
# Exercise: Implement ADDI on LC-2200 datapath

How many cycles and what control signals are required to implement ADDI on the LC-2200 datapath? Spend **5 minutes** tracing each cycle.



Anatomy of an I-type instruction.

 


Table 4: Register Selection Map

RegSelHi	RegSelLo	Register
0	0	RX (IR[27:24])
0	1	RY (IR[23:20])
1	0	RZ (IR[3:0])
1	1	unused

# Implementing ADDI

1. Load Ry into A
2. Load sign extended offset into B
3. Add A and B and store in Rx


## I-type instructions (addi, lw, sw, beq):

bits 31-28: opcode  
 bits 27-24: reg X  
 bits 23-20: reg Y  
 bits 19-0: Immediate value or address offset



Table 4: Register Selection Map


RegSelHi	RegSelLo	Register
0	0	RX (IR[27:24])
0	1	RY (IR[23:20])
1	0	RZ (IR[3:0])
1	1	unused

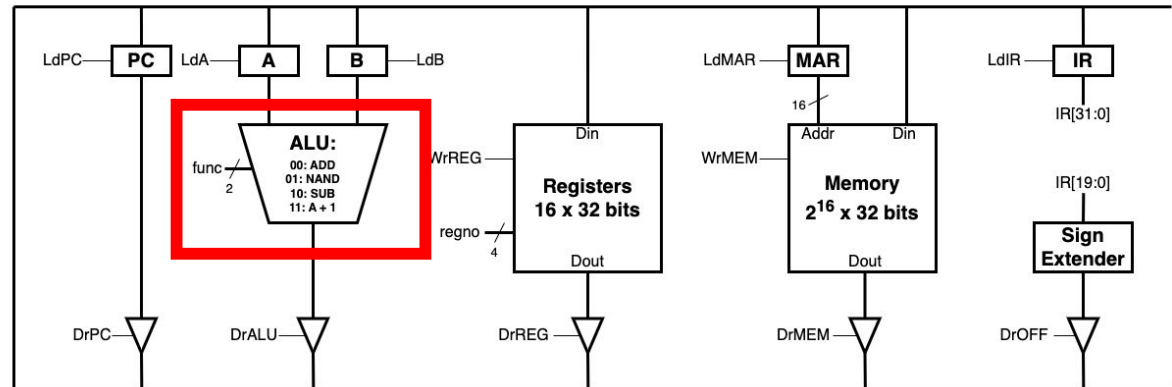




# ADDI Cycle 1: $R_y \rightarrow A$

What signals need to be asserted?

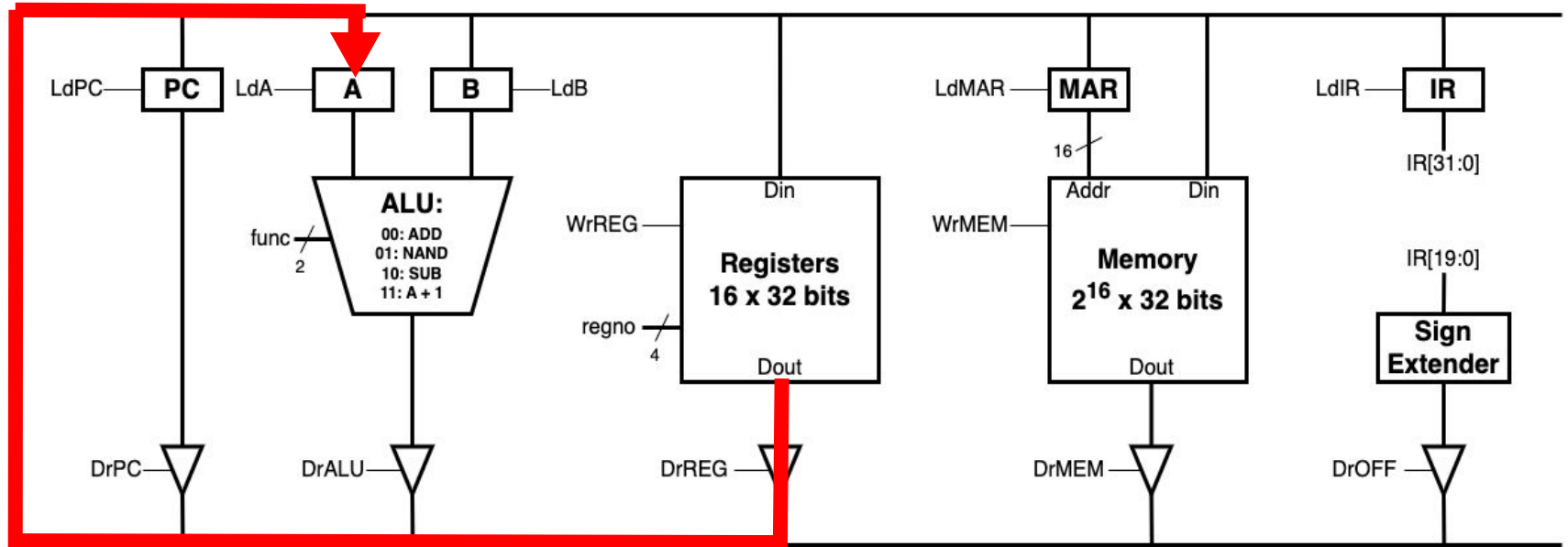


# ADDI Cycle 1: Ry → A

DrREG, LdA, RegSel = 01

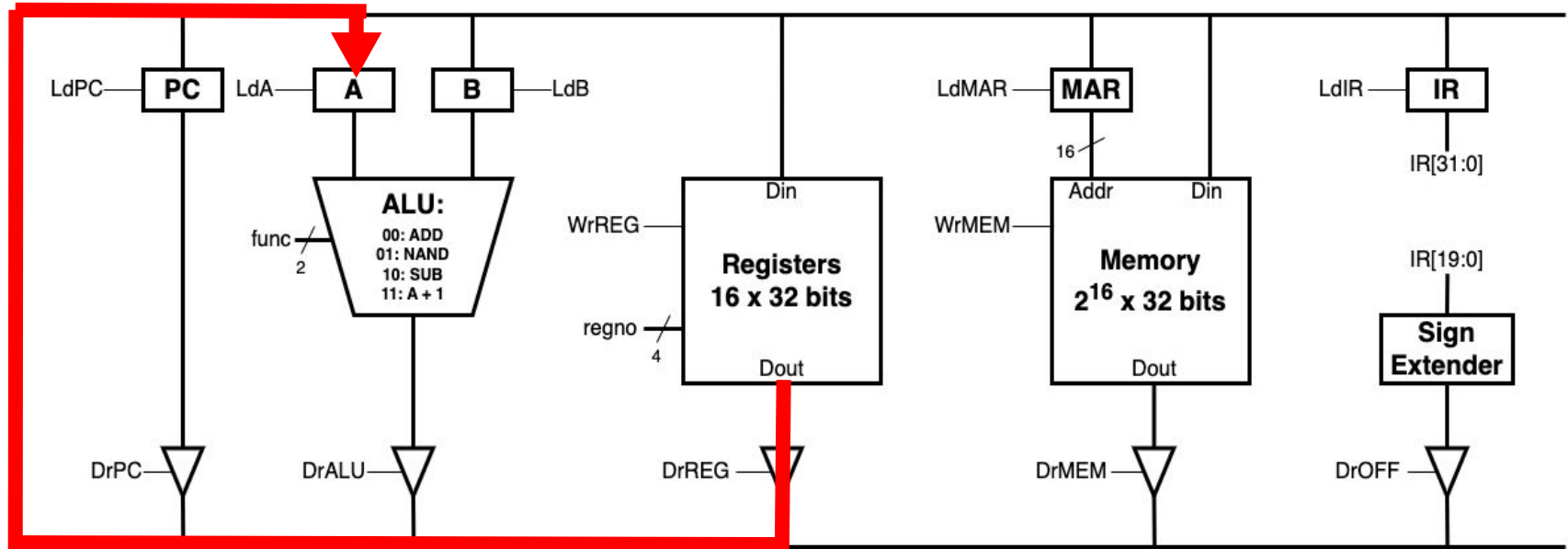


# ADDI Cycle 2: OFF → B

What signals need to be asserted?

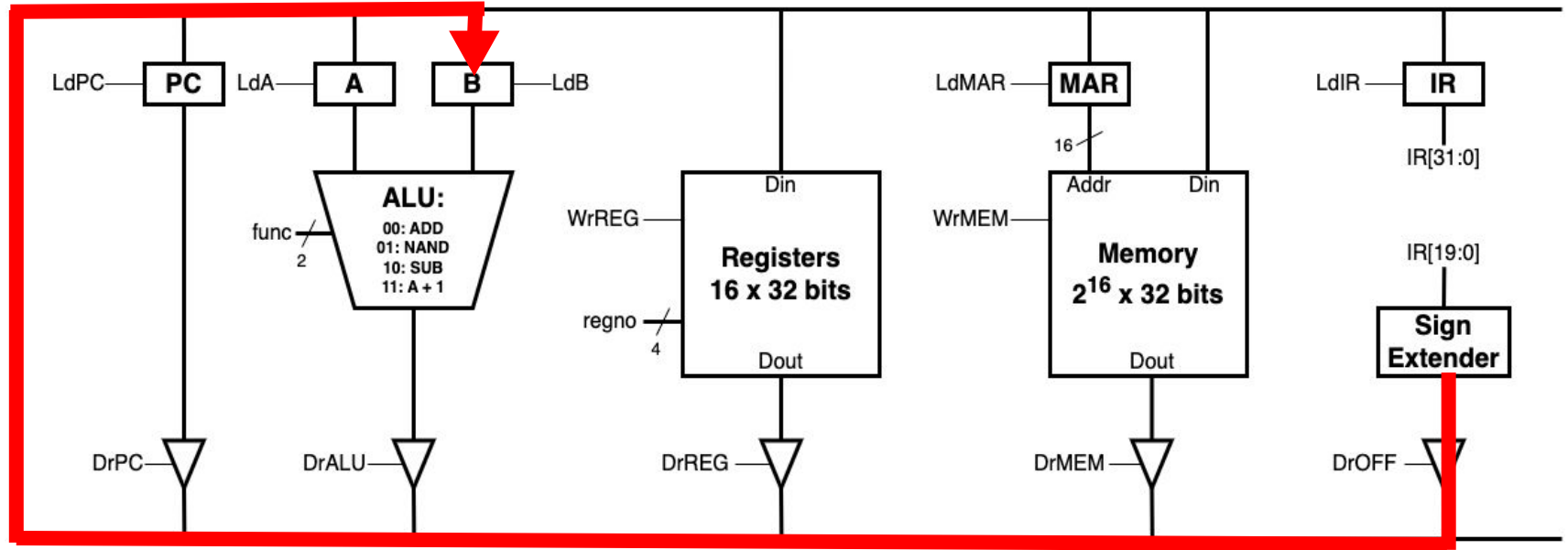


# ADDI Cycle 2: OFF → B

DrOFF, LdB

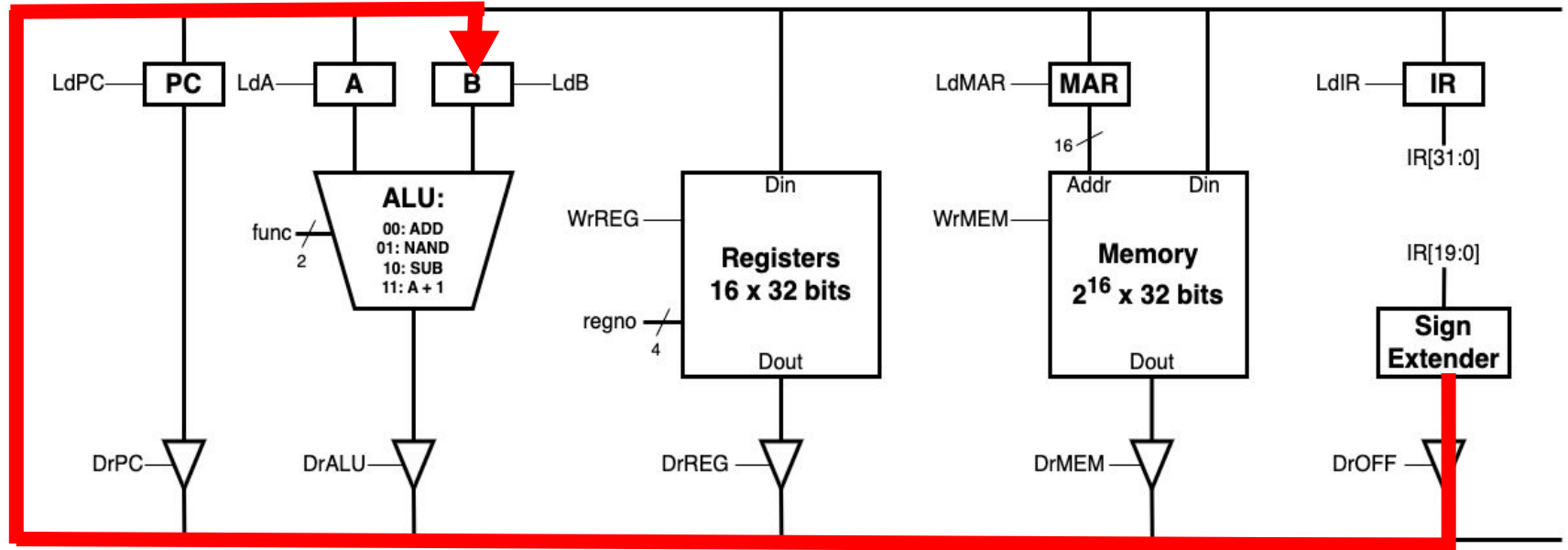


# ADDI Cycle 3: ALUout → Rx

What signals need to be asserted?

 

# ADDI Cycle 3: ALUout → Rx

func = 00, DrALU, WrREG, RegSel = 00

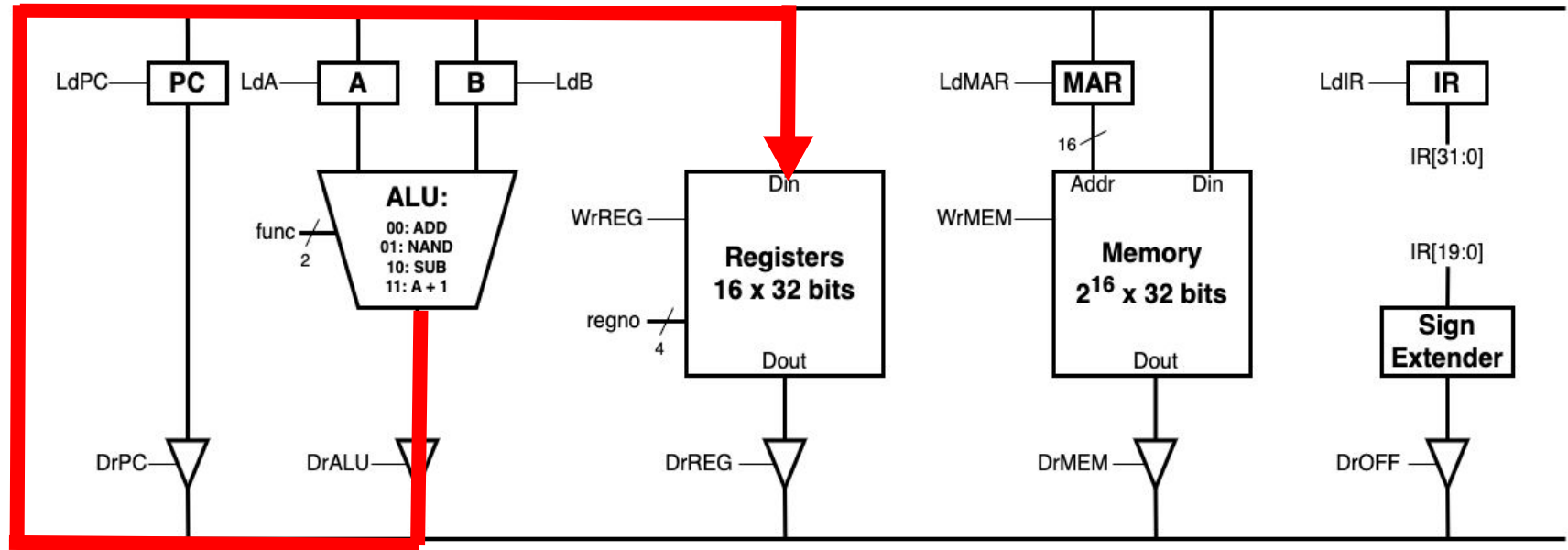

# Datapath Design


# Single vs. Double Bus Design

- **Single Bus Design**

- One bus wraps around the entire datapath
- Components take turns to orderly communicate
- More clock cycles per instruction

- **Double Bus Design**

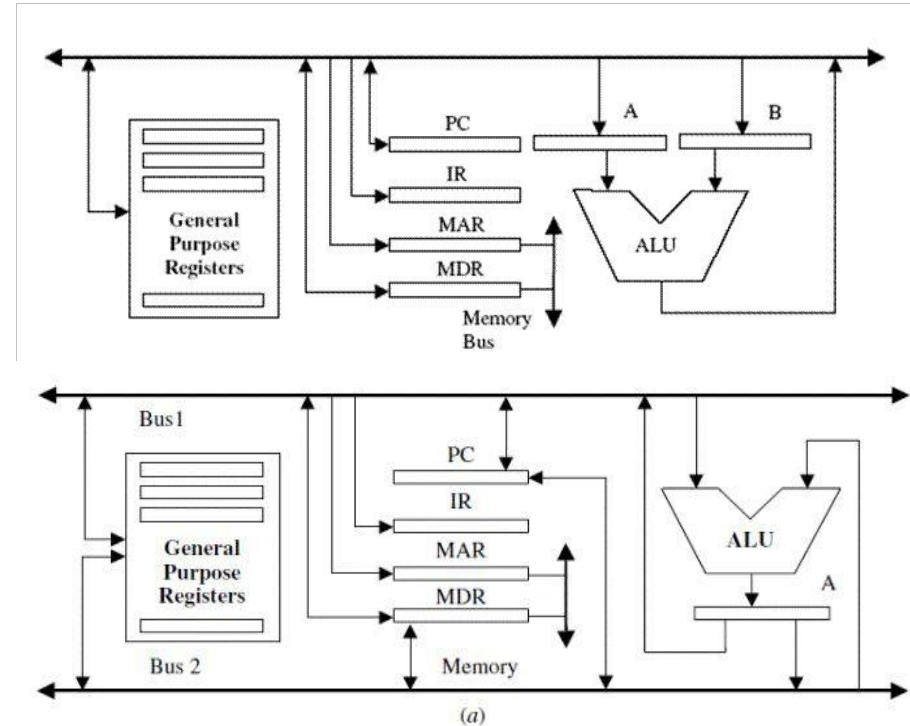- Two sets of bus wires.
- Two sets of data can communicate simultaneously.
- More hardware = greater price and heat






# The Power of 2 Buses: JALR example

Now in 1 cycle:

- $R_y \leftarrow PC + 1$
- $PC \leftarrow R_x$

DrPCBus1, LdReg,  
RegSelectIn = 01

RegSelectOut = 00,  
DrRegBus2,  
LdPC

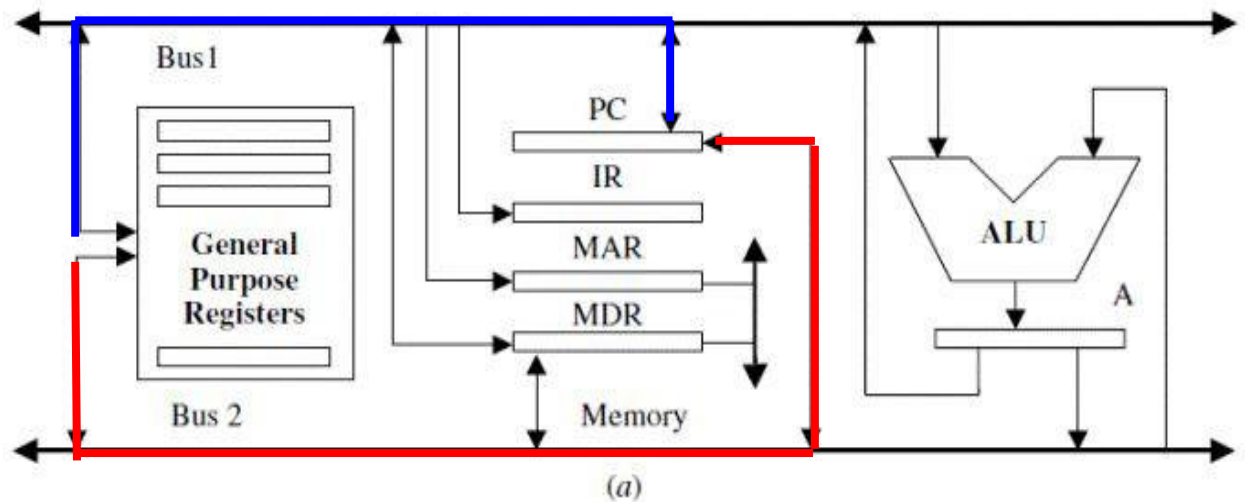

# Using the Bus

Regardless of bus design, we need the following for the datapath to work.

- **One component outputs data on one bus at one time.** Every other component will be listening to the output on that bus.
- We use tri-state buffers (bus drivers) to ensure that only one component is outputting to the bus at a time. **The tri-state buffers are hooked up to the DrX control signals.**
- We use the register “enable” input to ensure that only devices which want to store the data do so. **This is done using the LdXX control signals.**



# Single vs. Dual Ported Register File


Contains a collection of registers visible to the programmer.

- **Single Ported Register File**


- Allows for a single register read at a time
- The LC-2200 register file is single-ported!

- **Dual Ported Register File**


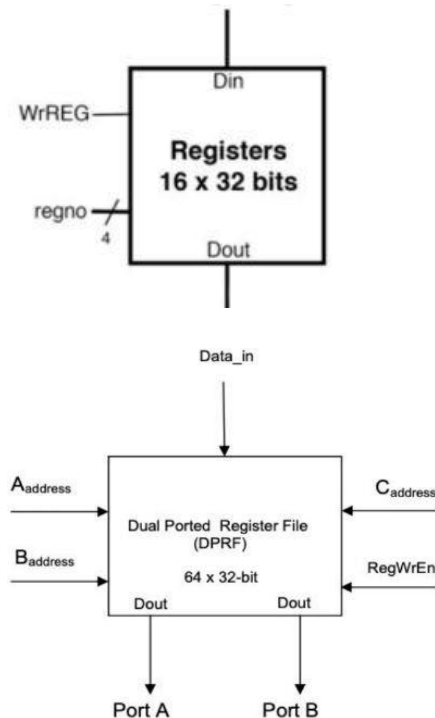
- Allows for two register reads at a time
- Requires additional address input
- Can still only write to one register at a time



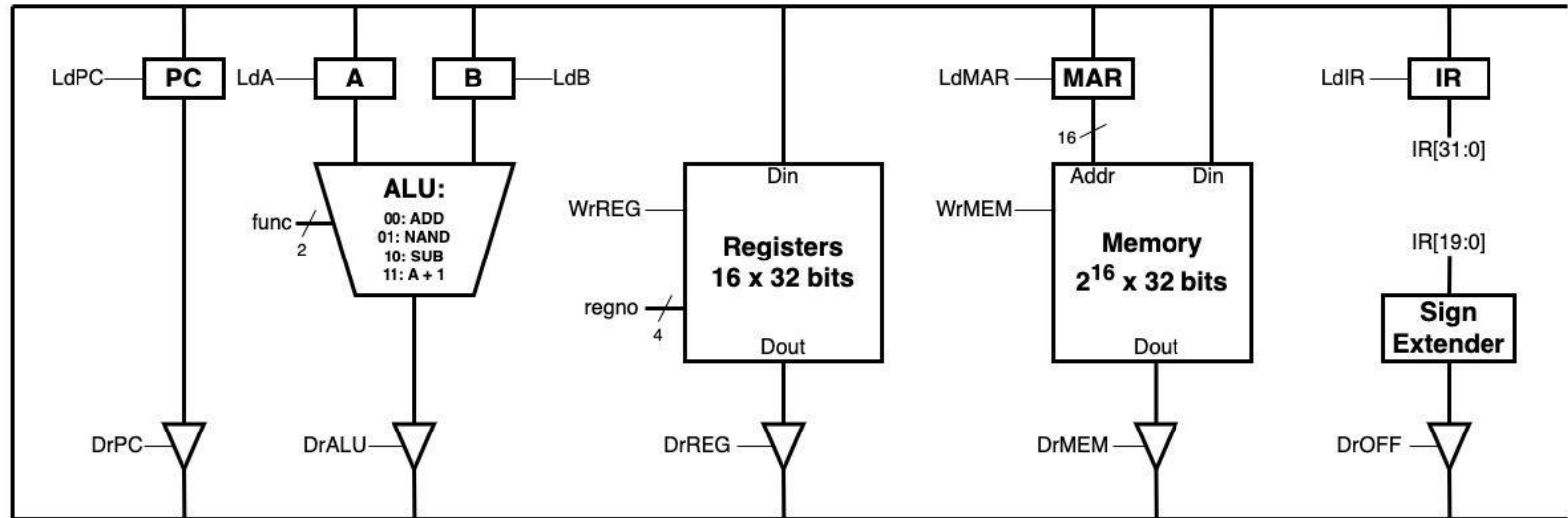**Exercise:** What changes would we have to make to the datapath to support a DPRF?



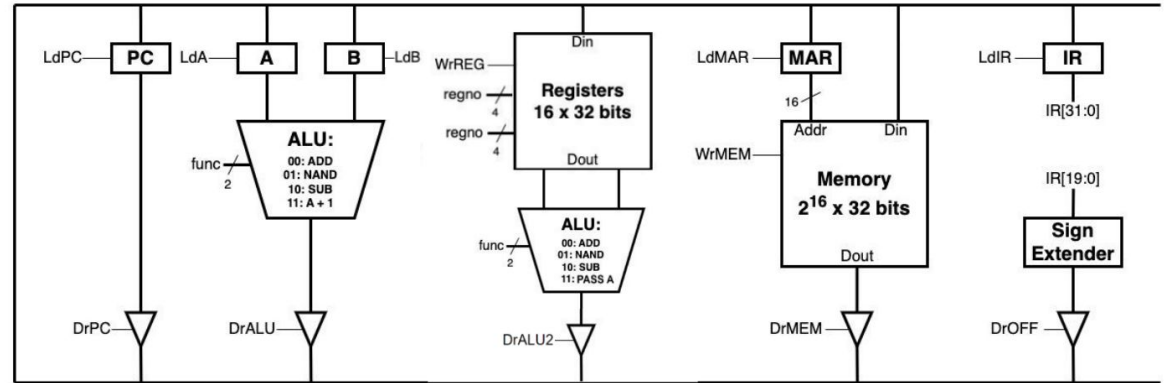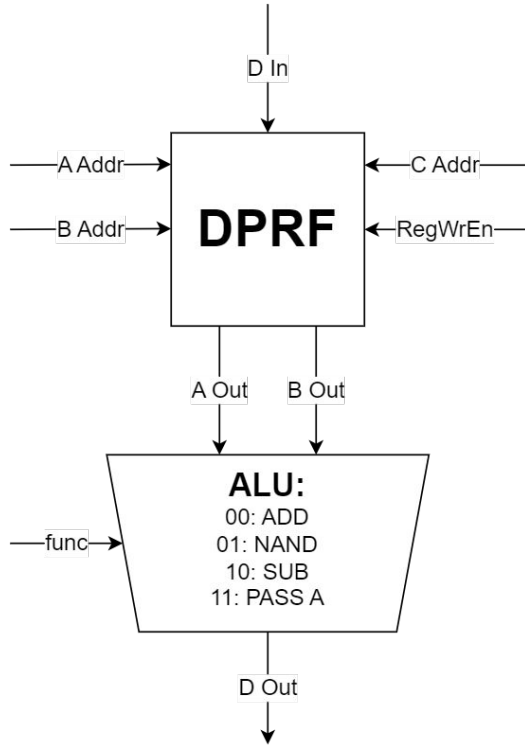**Answer:** Adding a 2nd ALU makes things work out!



2200

*Number of the day*

# Project 1 Q&A

**Thanks for attending!**